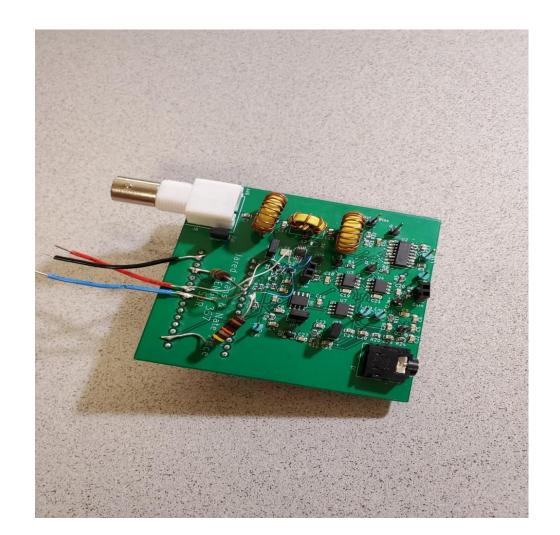



Software Defined Radio

Jared Evans and Nate Price


What is a Software Defined Radio (SDR)?

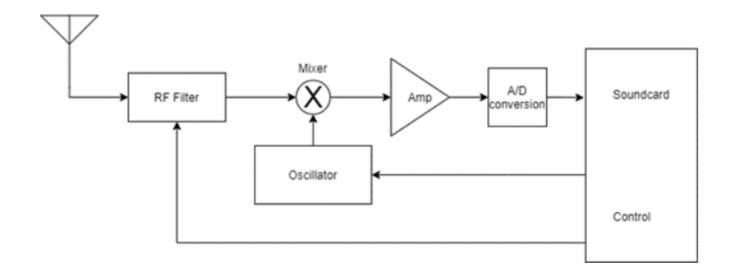• It is a radio receiver controlled by software implemented using an Arduino in the case of this project.






Block Diagram

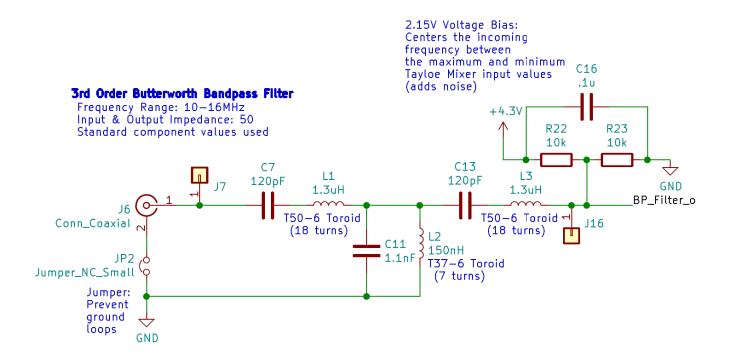


- Frequency Range: 10-16 MHz
- Based on Caleb Froelich and Konrad McClure's bandpass filter
- Values calculated using rf-tools.com

Bandpass Filter

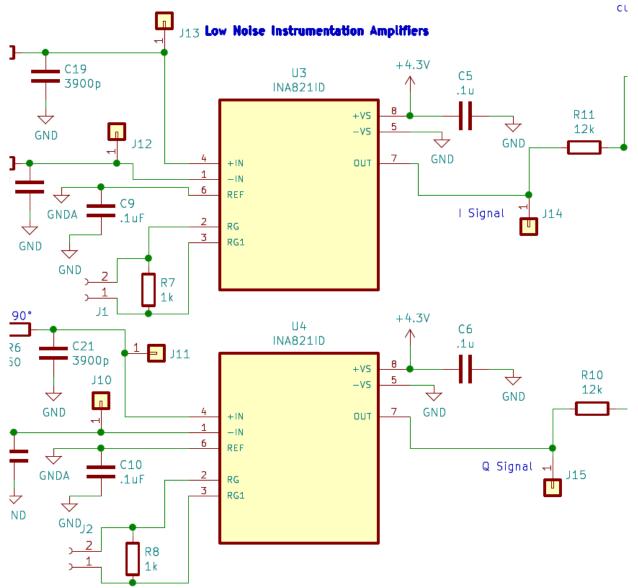


Instrumentation Amplifier

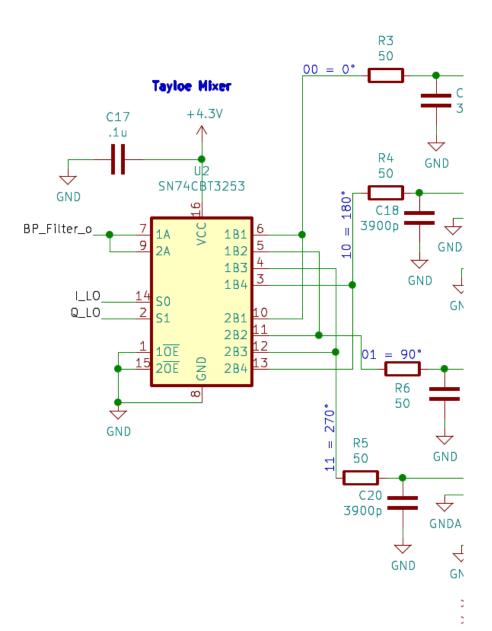

Tayloe Mixer

Voltage Smoother

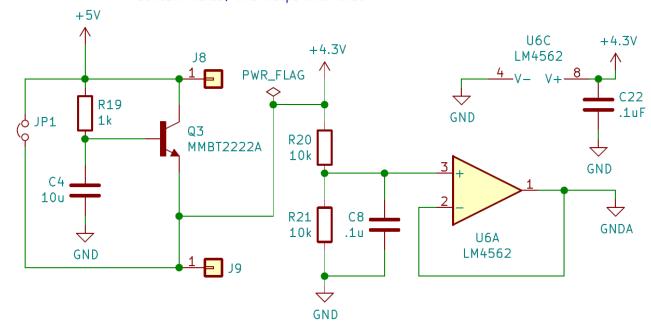The power supply from the USB may contain noise, this helps with that



- Based on Caleb Froelich and Konrad McClure's voltage smoother
- Modified to use an LM4562 op-amp

Voltage Smoother

Local Oscillator (Si5351a) Surface mount +3.3V low-cost **C3** 25 MHz crystal .1u \Diamond GND In this crystal, Y1 pins 2 & 4 CX3225 1 J17 go to ground, GND CLKO 10 but only pin 2 is displayed CLK1 9 I_LO +3.3V \triangle ___Q_L0 CLK2 6 GND GND 1 J5 U1 SCL_3V Si5351A-B-GT SDA_3V \triangle GND

• Originally incorrectly used resistors between +3.3V and ground

Local Oscillator

Converter - 5V to 3.3V The arduino nano uses 5V logic and the Si5351a uses 3.3 logic, this helps convert the voltages +3.3V+5VR16 R18 10k 10k 10k 10k SDA_3V SDA_5V BSS138 SCL_5V SCL_3V Q2 BSS138


- Design comes from Adafruit
- Originally incorrectly tried to use fewer resistors

Voltage Converter

Two Pole Sallen-Key Low Pass Filter Designed for a 100kHz cutoff frequency C25 100pF U7A R25 R11 LM4562 C28 12k 12k 10uF C23 100pF • J14 U7C +4.3VGND LM4562 \rightarrow .1uF GND GND 🕁 R10 R24 12k 12k C24 U7B LM4562 GND 🕁 C26 100pF


• Design based on and values calculated using http://sim.okawa-denshi.jp/en/OPseikiLowkeisan.htm

Lowpass Filter

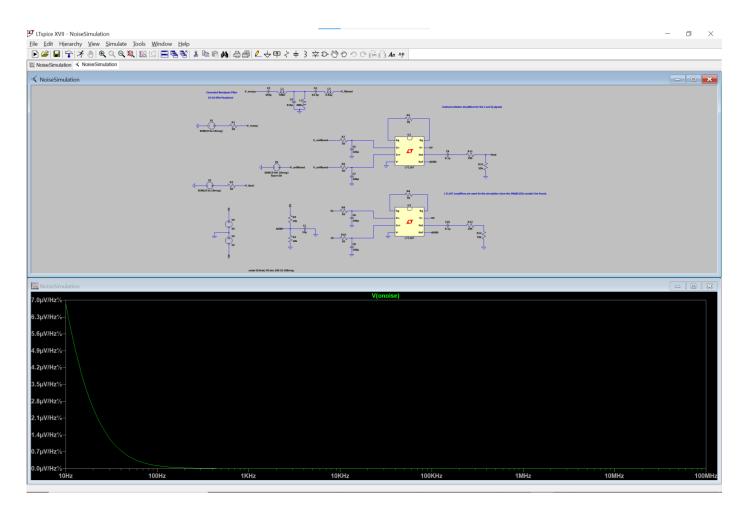


• This was one of our noise simulations

Simulations

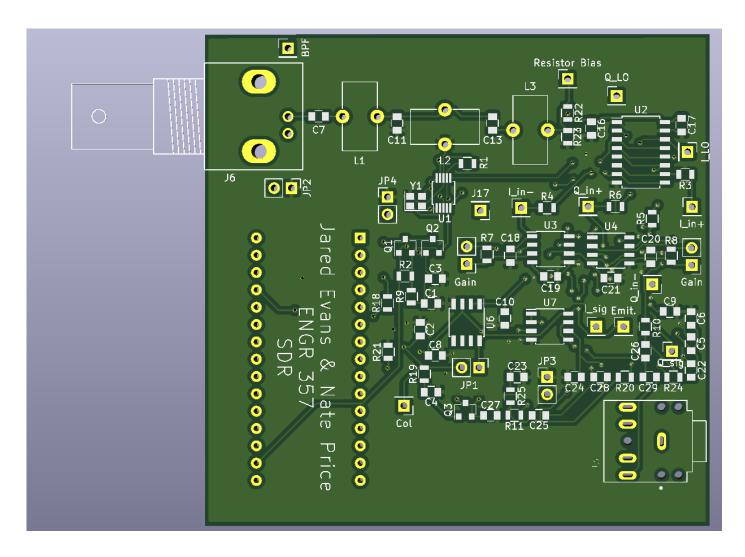


Tip: Check your PCB connections carefully!

PCB

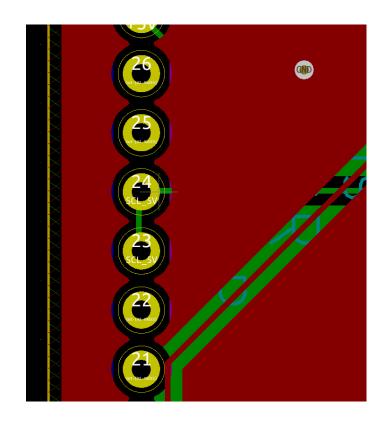

Errors Encountered

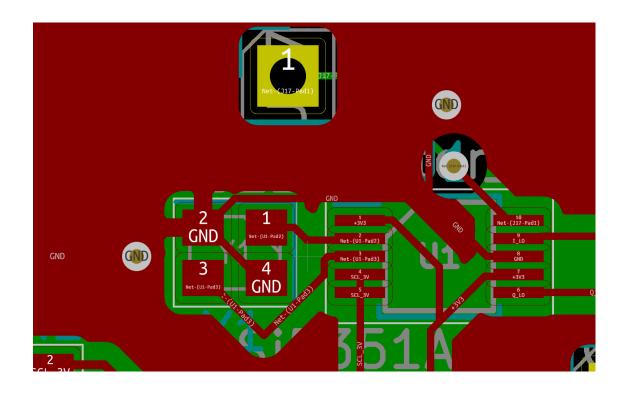


- The SCL and SDA pins on the Si5351 were shorted which led to several traces needing to be cut.
- · Another trace was cut but shouldn't have been.
- Several THT components are externally connected to correct these mistakes.


```
// This is for models that use the Si5351 to produce the I/\zeta
360
     unsigned long long pll freg;
361
     unsigned long long new freq = freq * 100;
362
     uint fast8 t mult;
363
364
     Serial.print("\nfreq:\n");
365
       Serial.print(new freq);
366 /
      // mult must be less than 128 (7 bits) according to document
367
368
     // mult of 50 only works for this frequency, needs to be cha
369
     mult = 50;
370
371
     pll freq = mult*new freq;
372
373
     si5351.set freq manual (new freq, pll freq, SI5351 CLK1);
374
     si5351.set freq manual (new freq, pll freq, SI5351 CLK2);
375
     // Now we can set CLK1 to have a 90 deg phase shift by enter
376
     // mult in the CLK1 phase register, since the ratio of the E
377
     // the clock frequency is mult.
378
     si5351.set phase(SI5351 CLK1, 0);
379
     si5351.set phase(SI5351 CLK2, mult);
380
     // We need to reset the PLL before they will be in phase ali
381
     si5351.pll reset(SI5351 PLLA);
382
383 #endif
```

359 #else

Software Issues

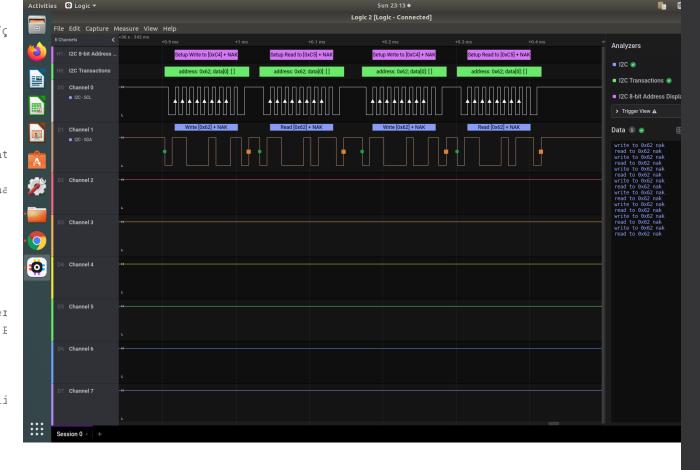

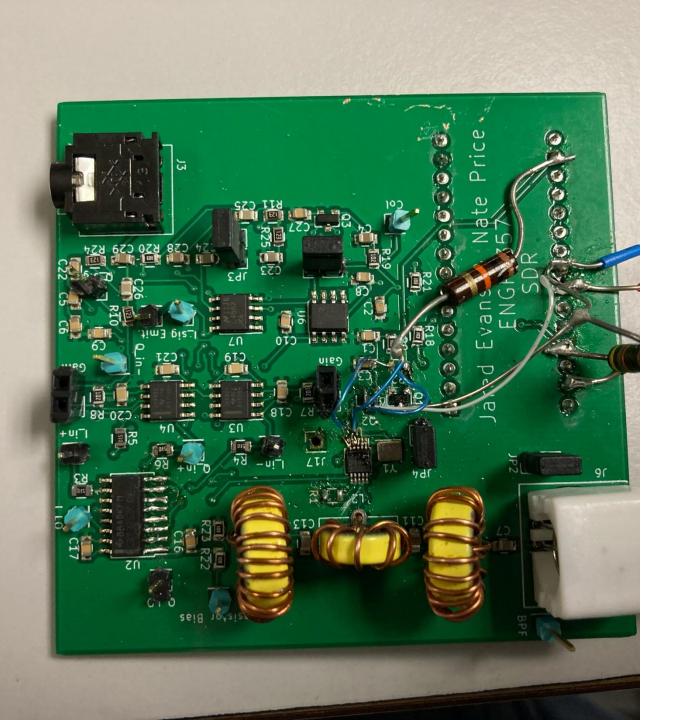- · Understanding how the use the logic analyzer
- · Making sure the correct I2C address was used/acknowledged
- Quisk configuration settings
- Frequency used to set the phase with the Si5351Arduino library needed to be multiplied by 100
- Some code needed to be reconfigured to work with clocks 1&2 instead of clocks 0&1




Results – Nate's Board

- I2C address 0x62 "nak"
- Would need to replace the FET where many soldering fixes were made
- Best ways to fix it:
 - Design a new PCB, have it made, solder everything again
 - Use one of the extra broken PCB's to start again, knowing which fixes are needed
- Either way requires a lot of time desoldering and then soldering again
- Ultimately decided to make sure Jared's board worked



Results – Jared's Board

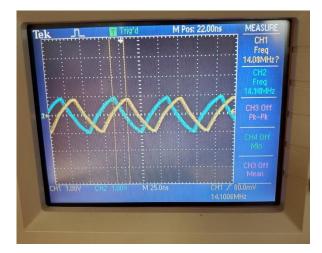- Si5351 communicates with Arduino
- Able to set phases
- Really good sensitivity (< 0.1 uV)
- · Quisk able to pick up signal from the antenna





Video

It's a bit difficult to see on the video, but the frequency running when this video was being recorded was 14.2787 MHz. Also, while it's a little hard to hear, we could hear someone who sounded like he was asking about practicing law in a "public sense".

Lessons Learned



Put in the effort into understanding circuits designed by others



Check the PCB (and everything else) carefully!



Collaborate as much as possible



Get as much software as possible configured early



Questions